
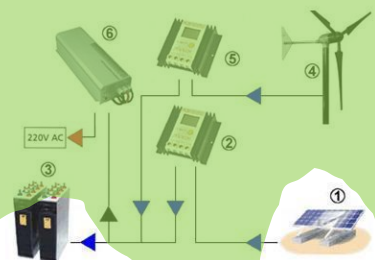

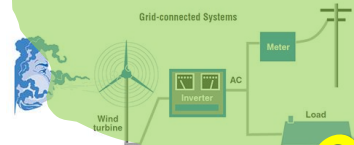
# POWER INJECTION TO THE GRID Grid Tie Inverters



- ① Grupo de módulos fotovoltaicos
- ② Regulador de carga solar
- ③ Grupo de acumuladores
- ④ Aerogenerador
- ⑤ Regulador electrónico de carga
- ⑥ Inversor 12 V cc - 220 V ac

Manuel Rico-Secades June 17, 2015



SECRETARÍA DE EDUCACIÓN PÚBLICA



ESTADOS UNIDOS MEXICANOS

TECNOLÓGICO NACIONAL DE MÉXICO  
Centro Nacional de Investigación y Desarrollo Tecnológico

"2015, Año del Generalísimo José María Morelos y Pavón"



**cenidet**  
Centro Nacional de Investigación y Desarrollo Tecnológico


**1er Taller de Aplicaciones de Electrónica de Potencia en el Manejo de Energías Renovables**  
Cuernavaca, Morelos, 19 de junio de 2015

**ORGANIZADOR:**  
Centro Nacional de Investigación y Desarrollo Tecnológico - CENIDET



**EXPOSITORES:** Universidad de Oviedo, España, IJASLP, ITES, I.T. de Celaya, I.T. de Herposillo, Tecnológico de Soconusco, I.T. de Chihuahua, y el CENIDET.  
Con el apoyo de FOMEX CONACYT - Gobierno del Estado de Morelos

Dr Manuel Rico-Secades  
EPI-GIJON  
Universidad de Oviedo

Cenidet – Mexico  
June 24, 2015

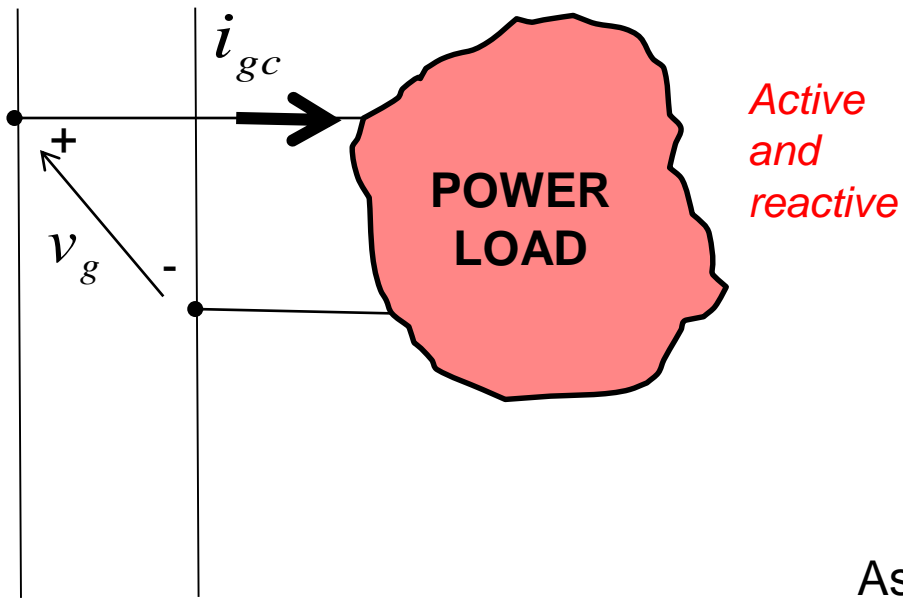

Valores eficaces

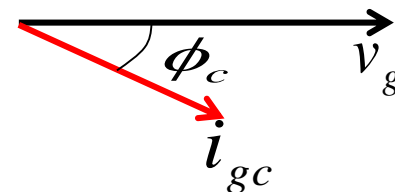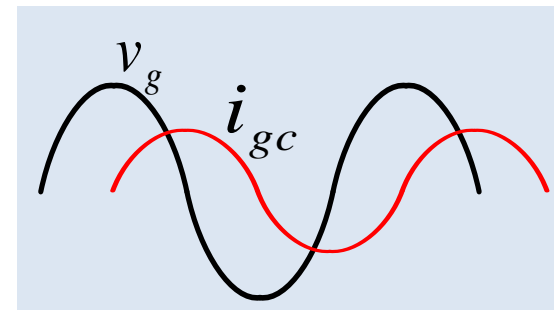

Inductive load

Assuming sinusoidal waveforms




POWER LINE

$$P = v_g \cdot i_{gc} \cdot \cos\phi_c$$

Active Power

$$Q = v_g \cdot i_{gc} \cdot \text{sen}\phi_c$$

Reactive Power

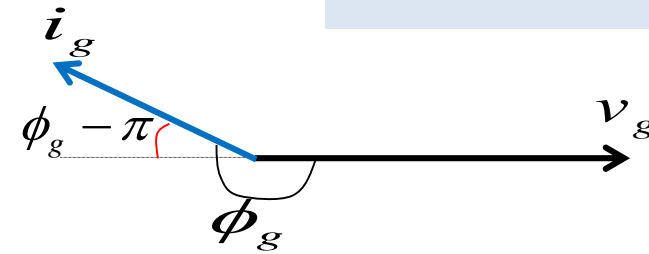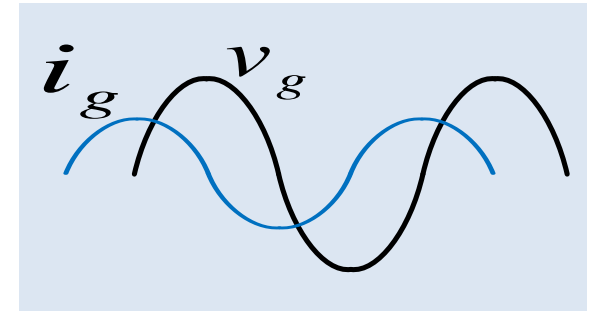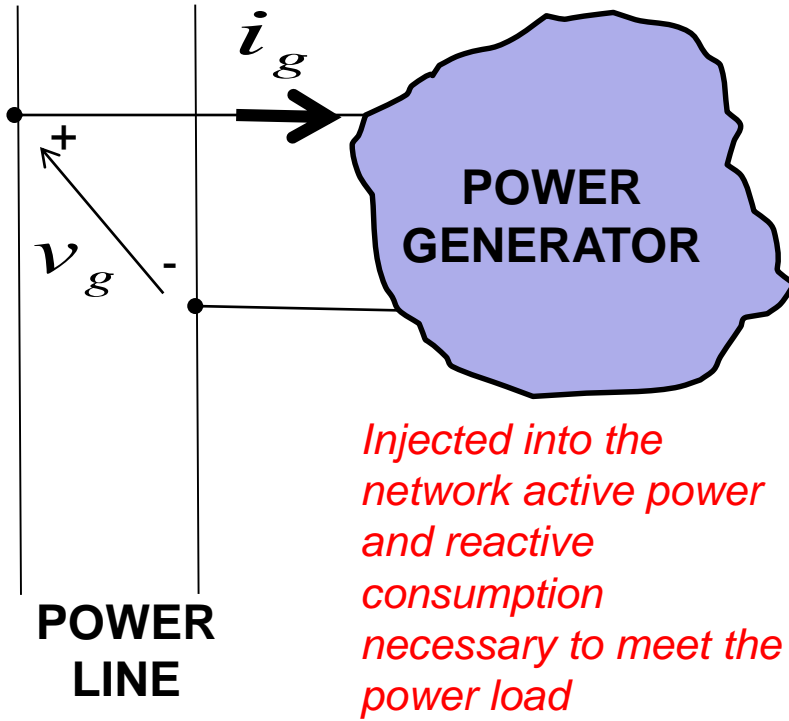

Active power generated


$$P = v_g \cdot i_g \cdot \cos(\phi_g - \pi)$$

Reactive power generated



$$Q = v_g \cdot i_g \cdot \text{sen}(\phi_g - \pi)$$

(Reactive power injected is capacitive)

# BASIC CONCEPTS

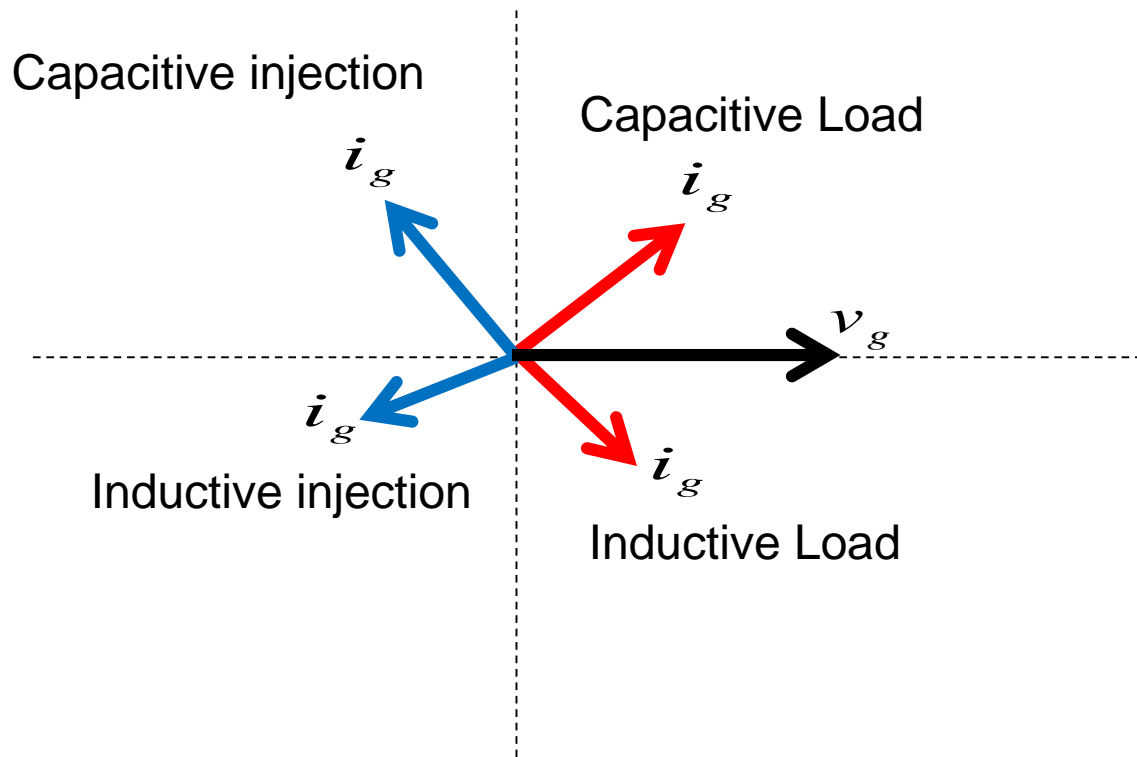


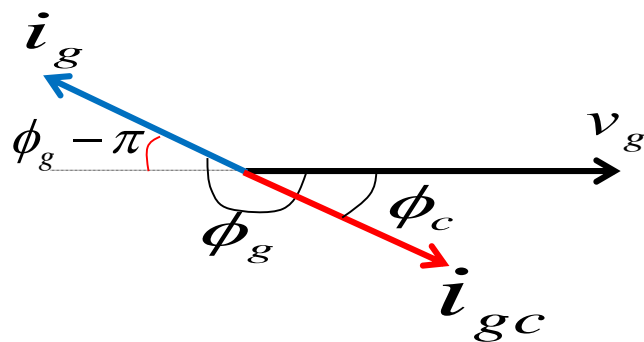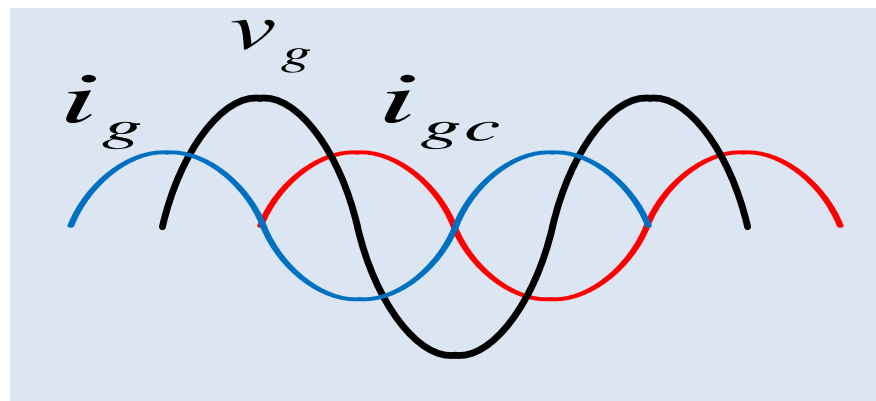***Our objective is to generate active and reactive power needed by a given load***



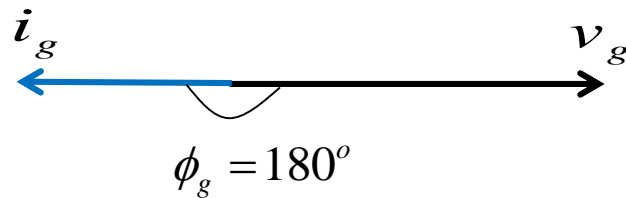
## SPECIAL SITUATIONS


Injecting only active  
 power  
 ( $Q=0$ )



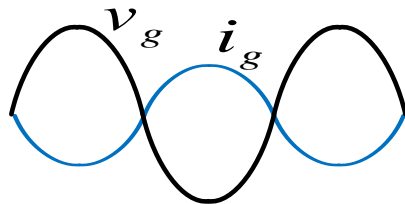
*Generation system behaves like a  
 resistance*



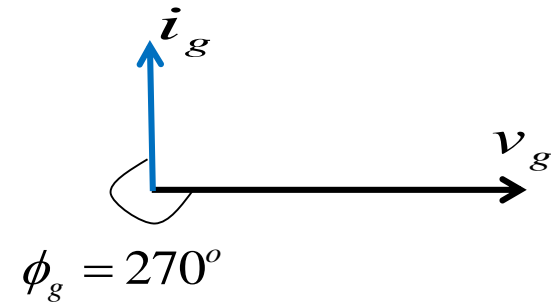
Injecting only  
 reactive power  
 ( $P=0$ )



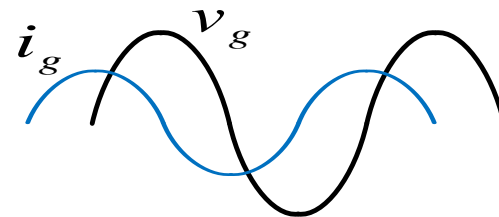
*Generation system behaves like a  
 capacitor*



# BASIC CONCEPTS

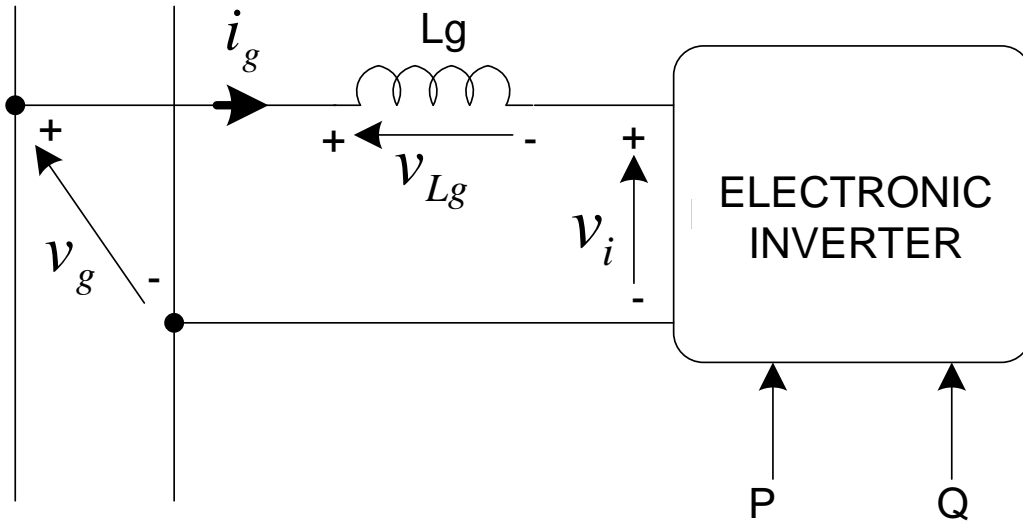


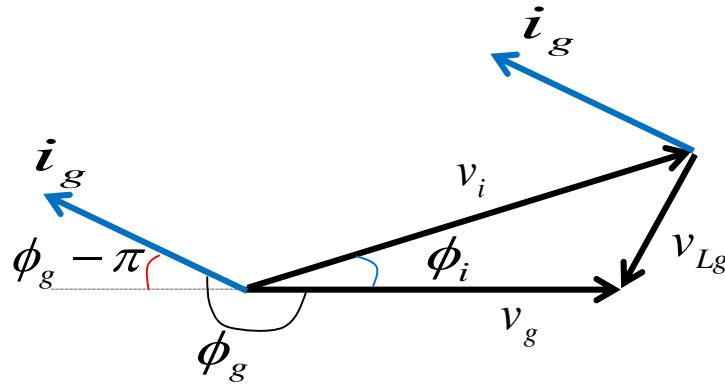Current  $i_g$  in delay  $90^\circ$  with voltage  $v_{Lg}$




# BASIC CONCEPTS

Active Power  
 (Q=0)

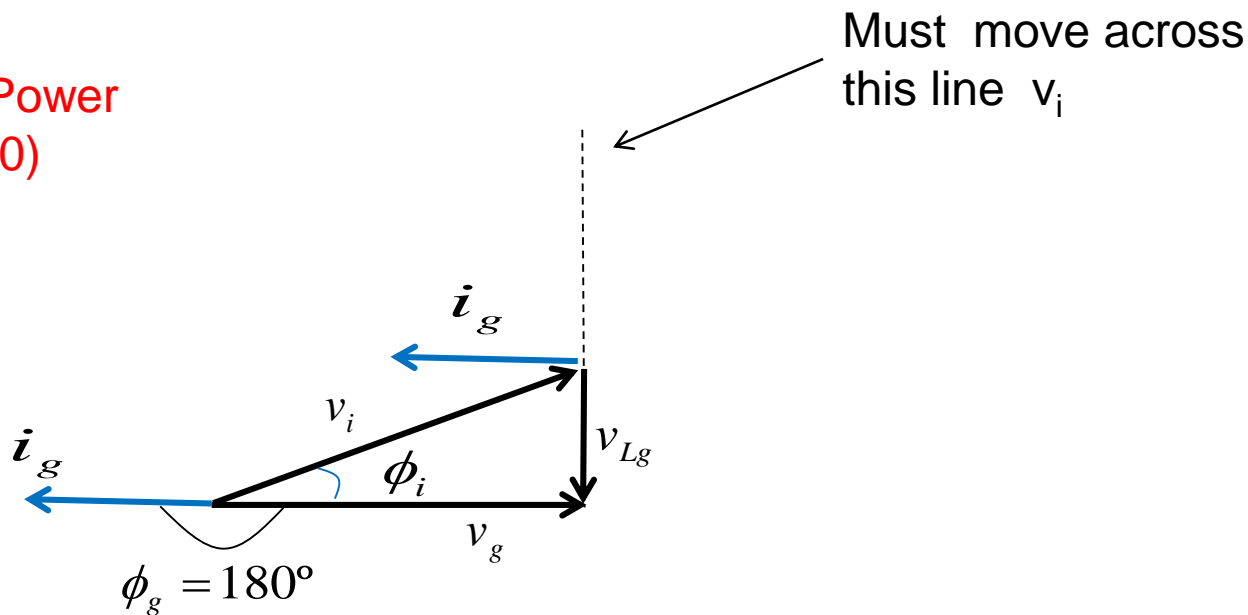


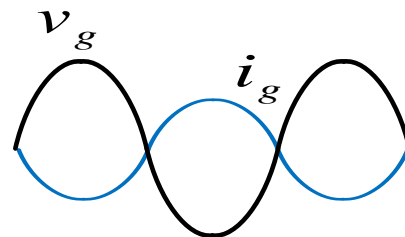System behaves like a negative resistance







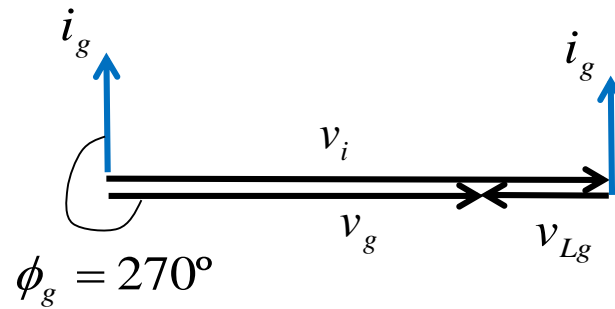Injecting only  
 reactive power  
 ( $P=0$ )




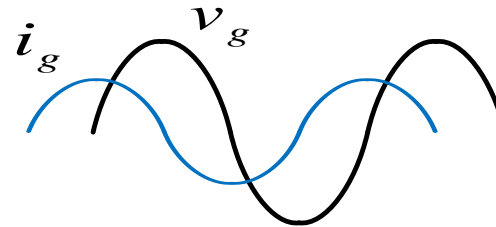
Generation system behaves like a capacitor



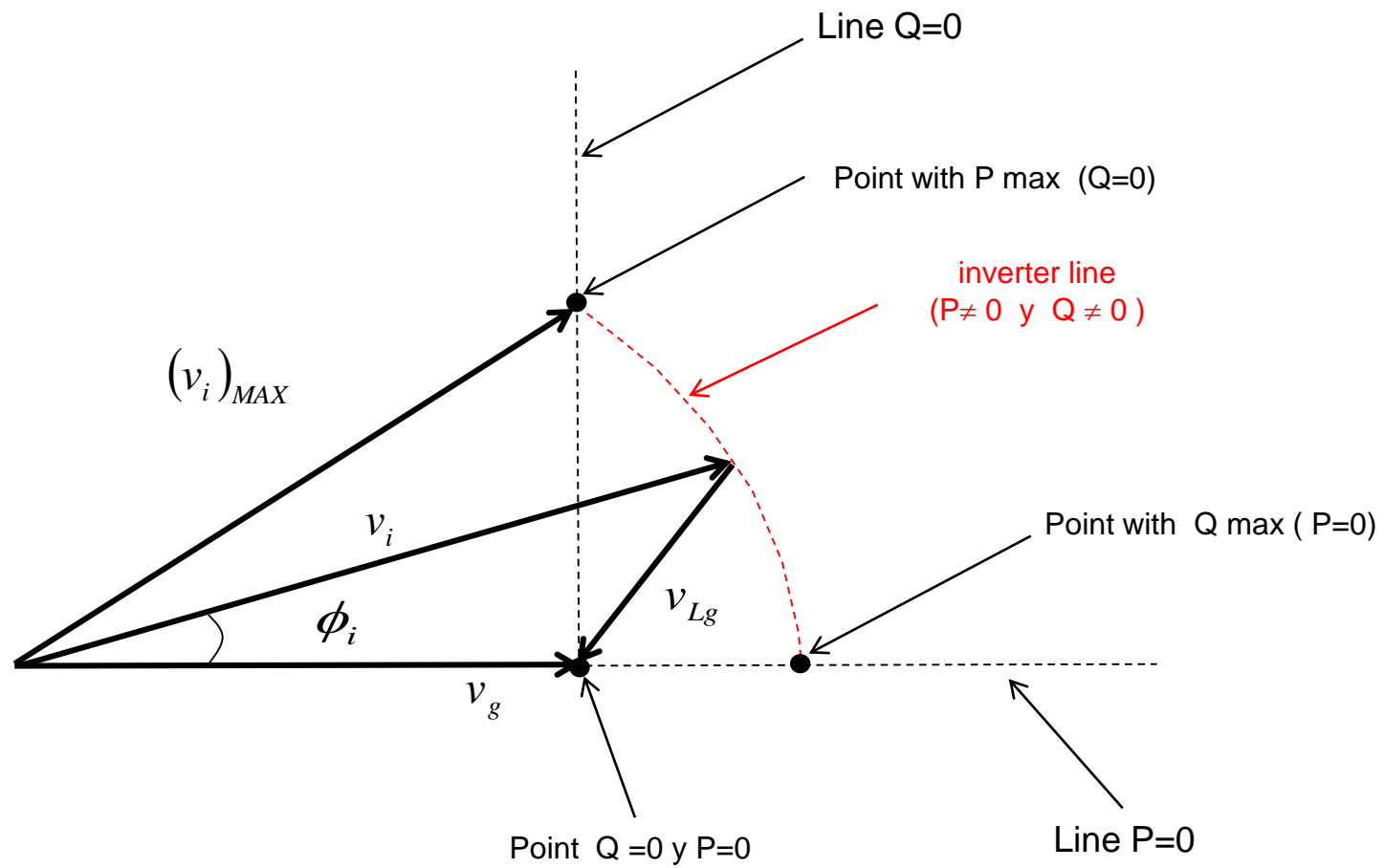


# BASIC CONCEPTS

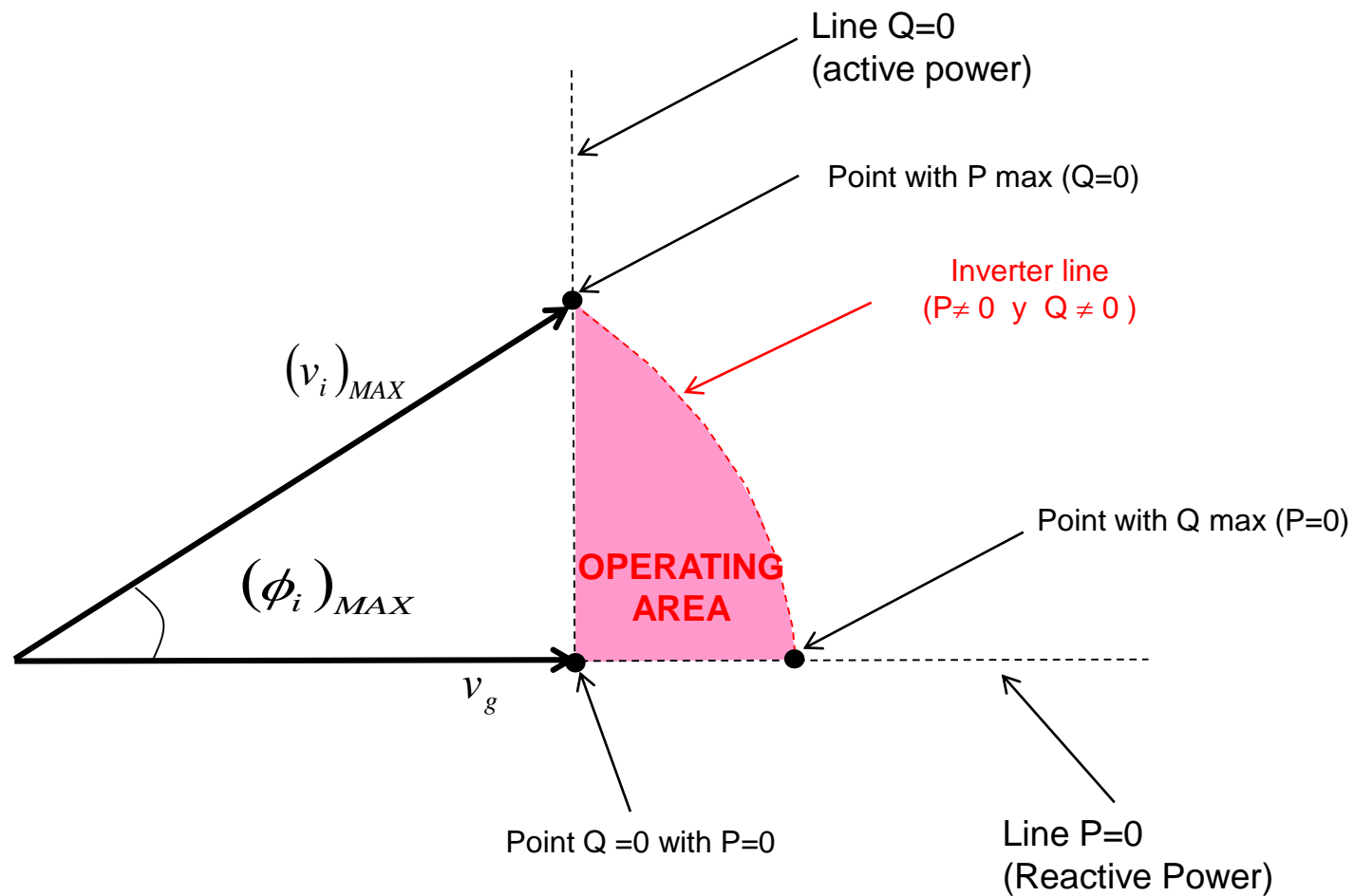


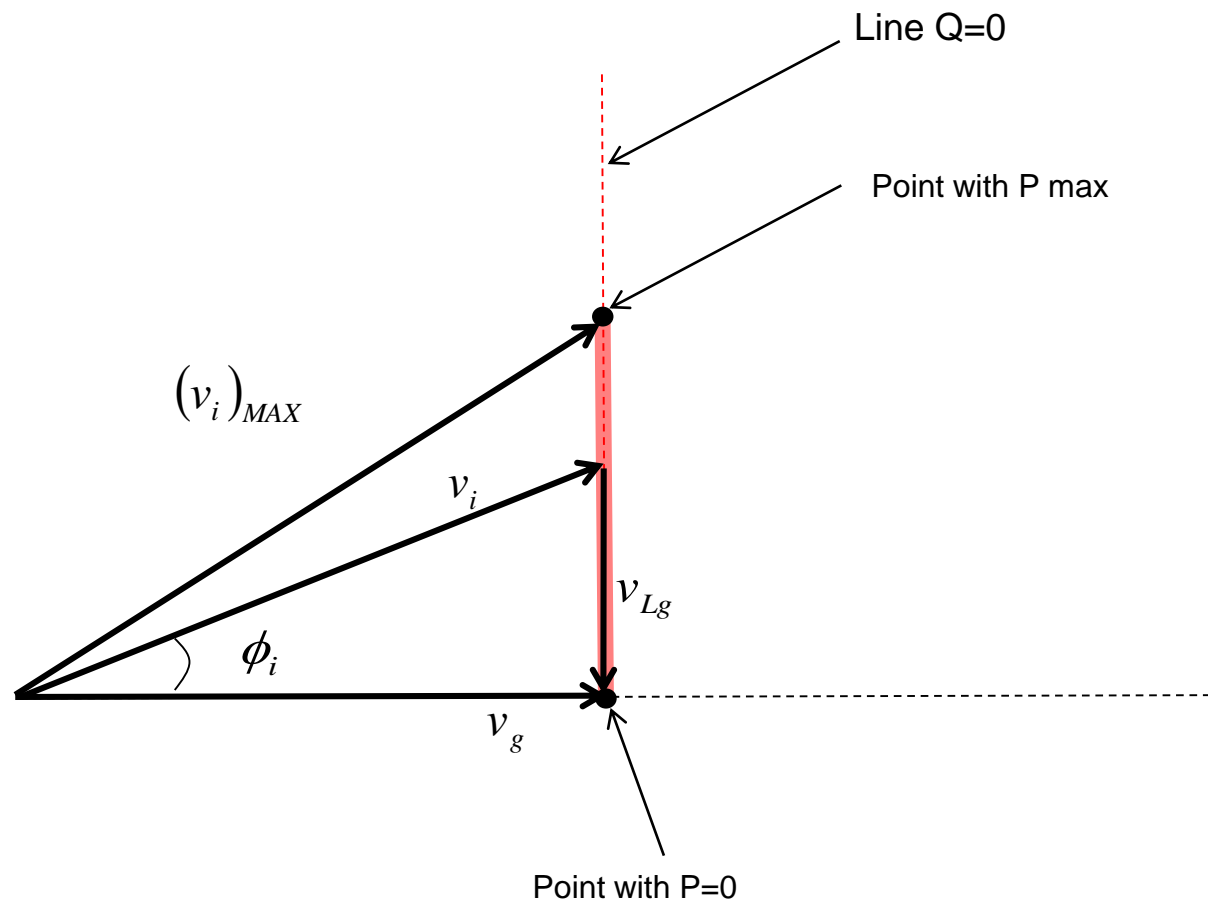


## ONLY ACTIVE POWER

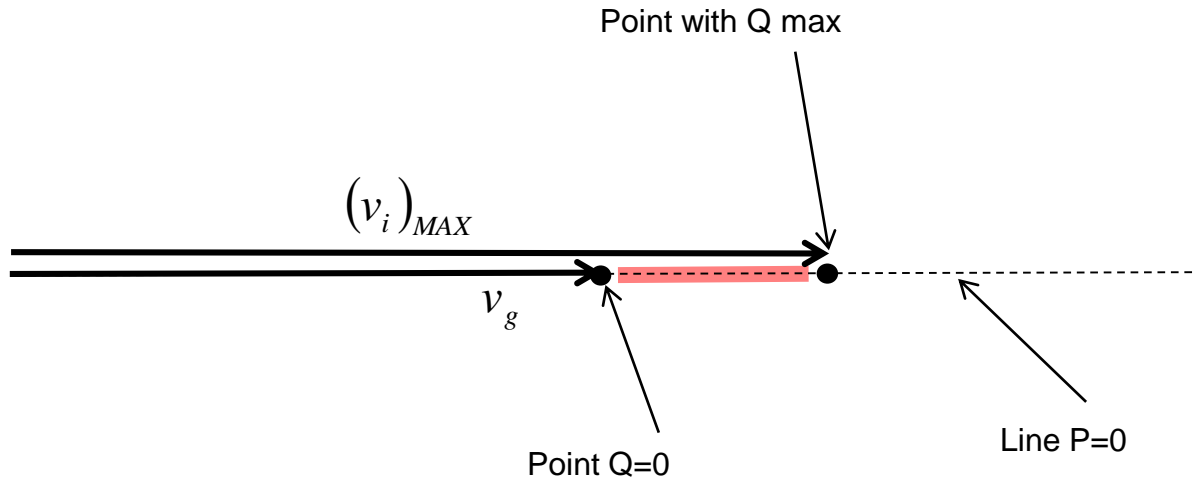

## ONLY REACTIVE POWER

## RESISTIVE BEHAVIOUR (PF = 1)

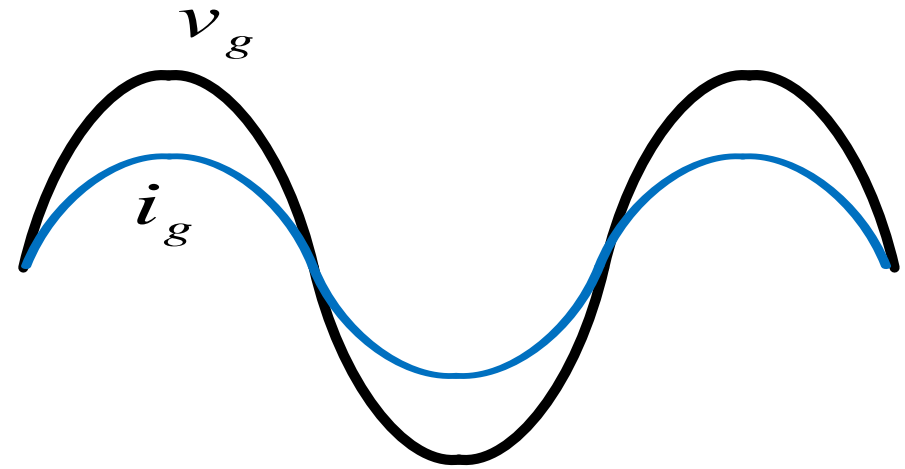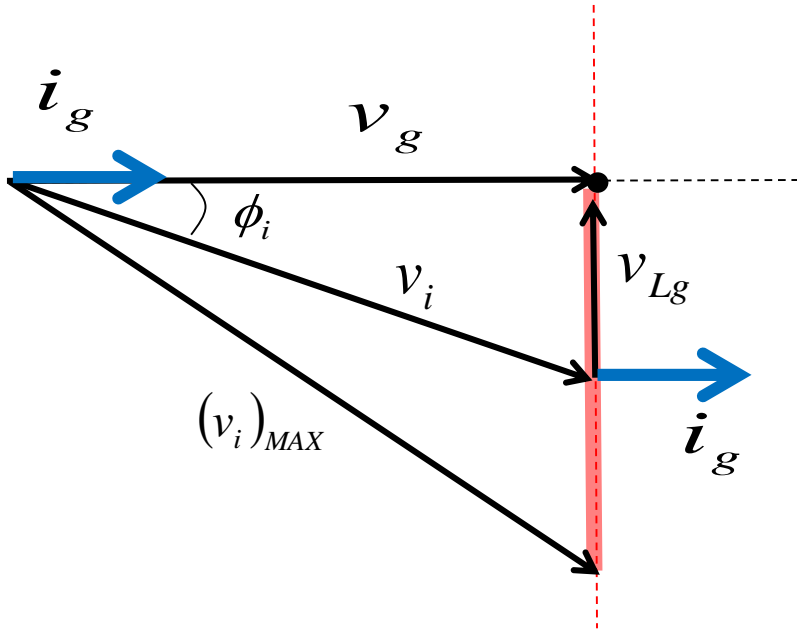


ACTIVE LOAD

Power Factor Correction

# Animation


# SINGLE-PHASE INVERTERS

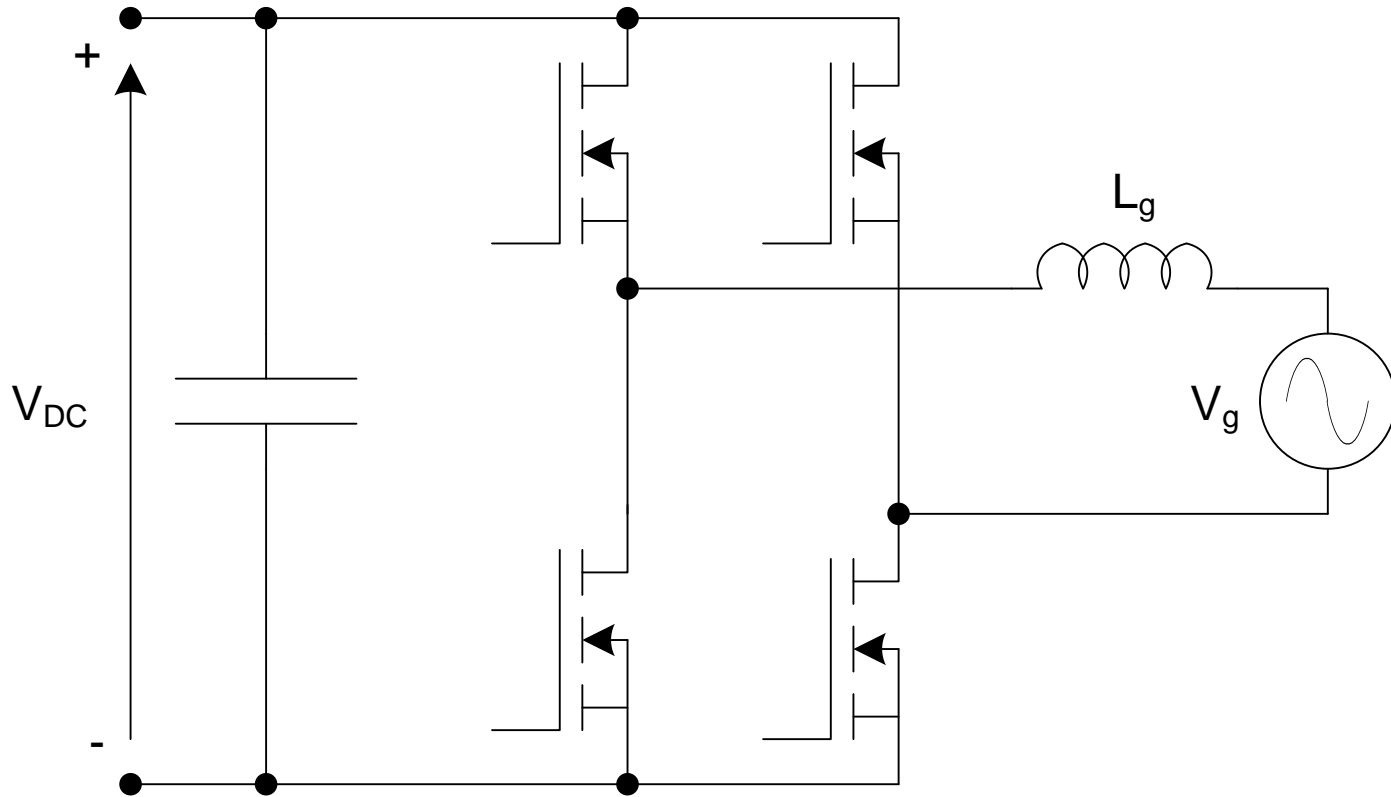

**FULL BRIDGE**




# SINGLE-PHASE INVERTERS

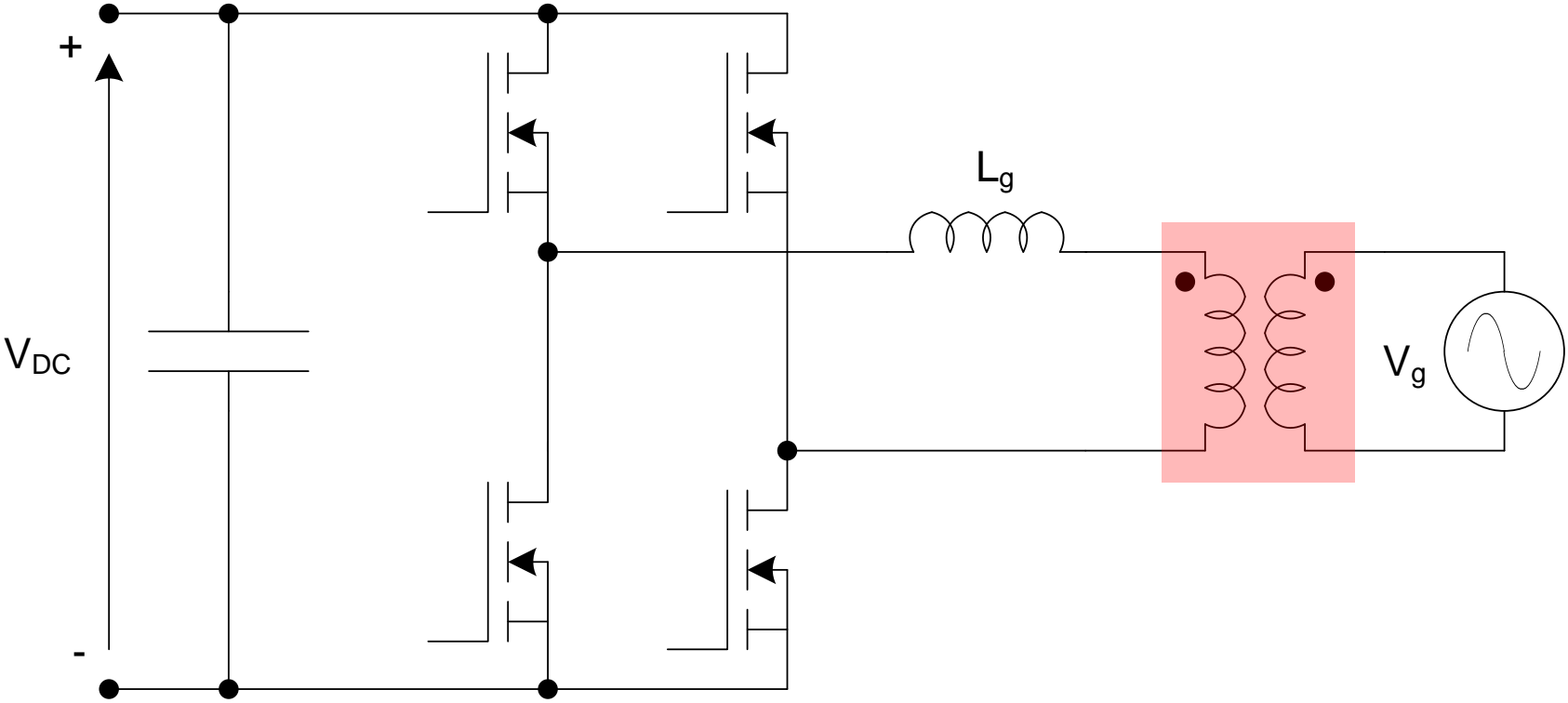


**ISOLATED FULL-BRIDGE**

# SINGLE-PHASE INVERTERS

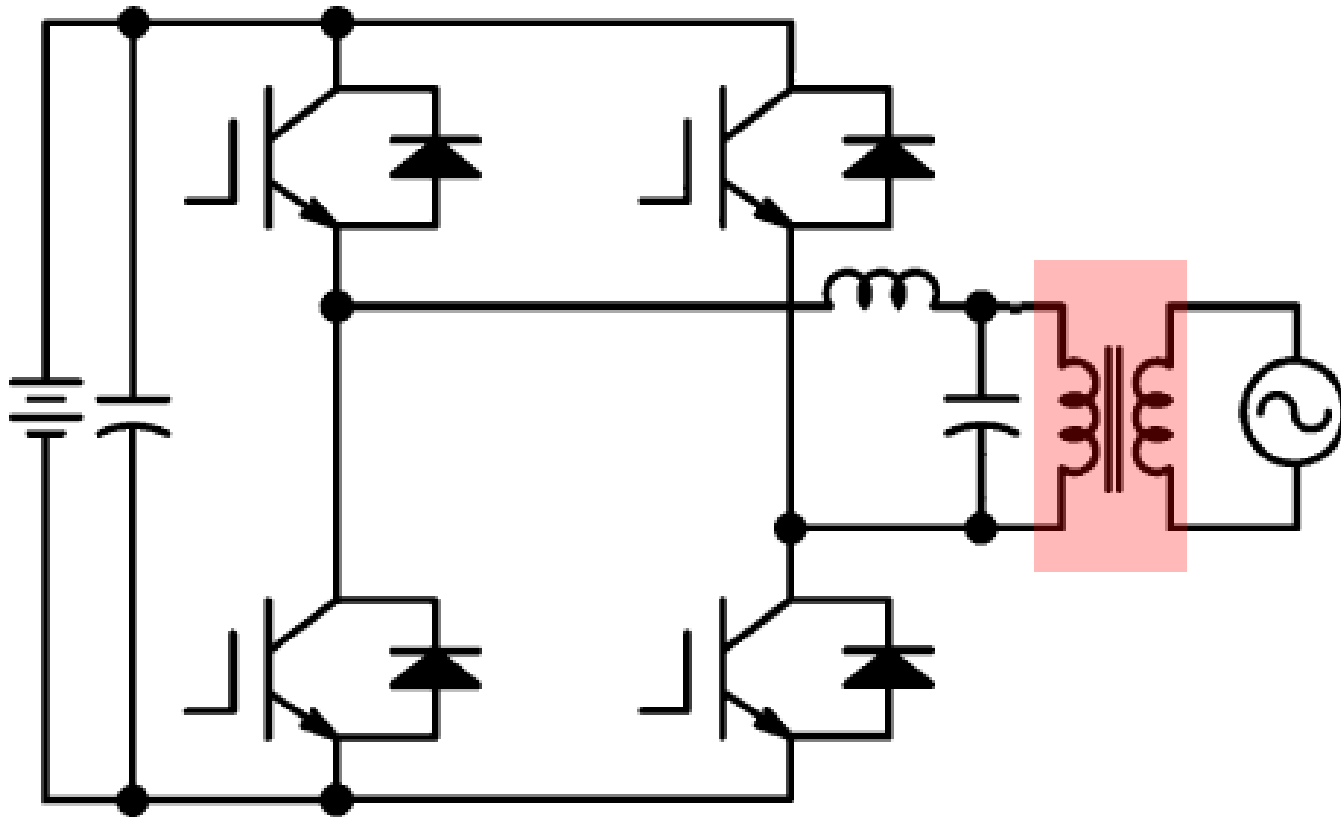

Traditional buck inverter and line-frequency transformer.

# SINGLE-PHASE INVERTERS

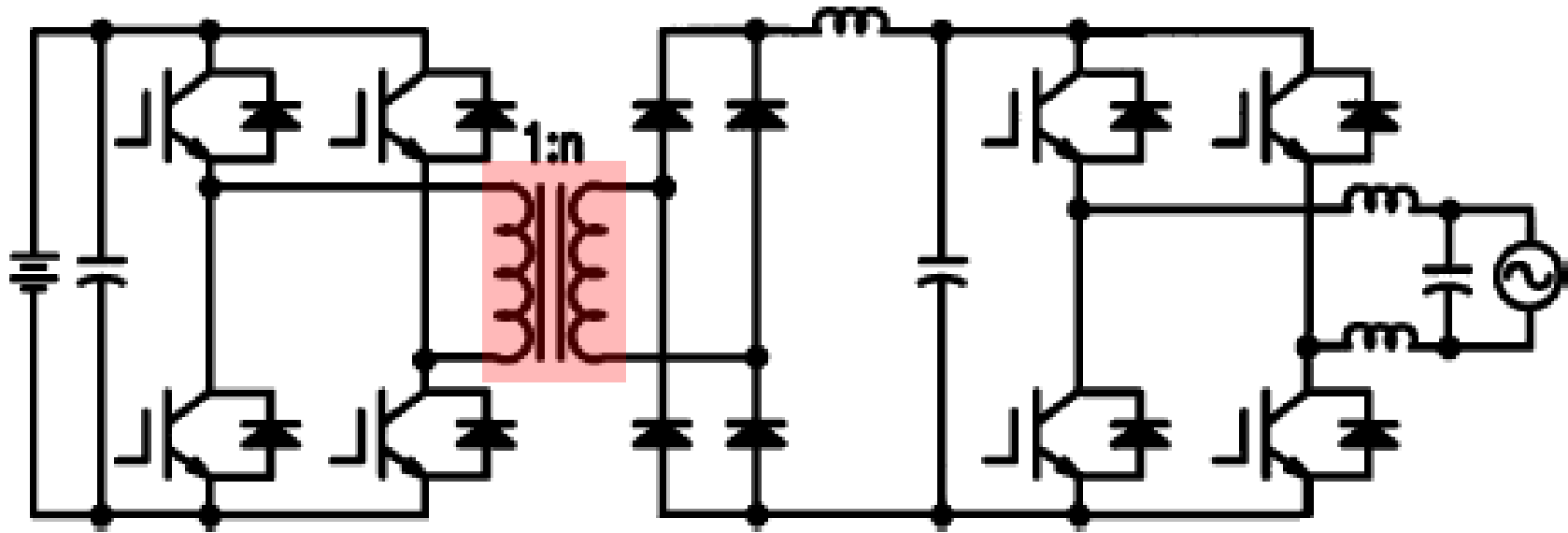

Multiple-stage inverter with a high frequency transformer.

Remus Teodorescu  
Aalborg University, Denmark

Marco Liserre  
Politecnico di Bari, Italy

Pedro Rodriguez  
Technical University of Catalonia, Spain


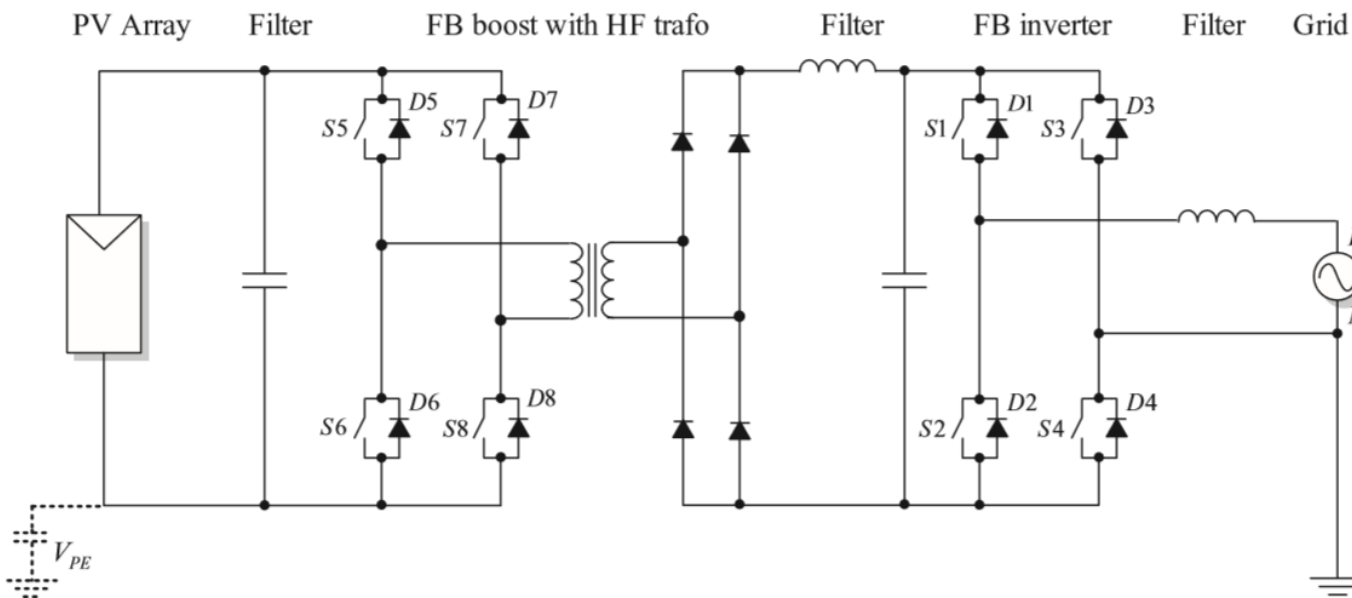


Figure 2.19 Boosting inverter with a HF transformer based on the H-bridge

# SINGLE-PHASE INVERTERS

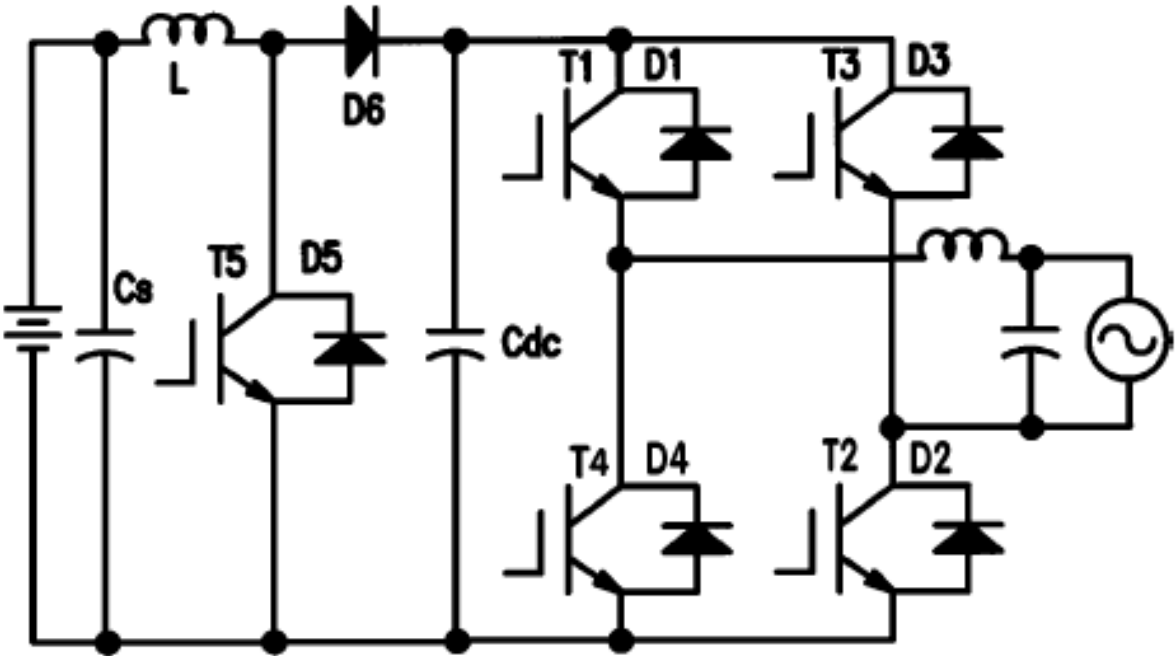


Two-stage boost inverter

**Remus Teodorescu**  
 Aalborg University, Denmark


**Marco Liserre**  
 Politecnico di Bari, Italy

**Pedro Rodriguez**  
 Technical University of Catalonia, Spain

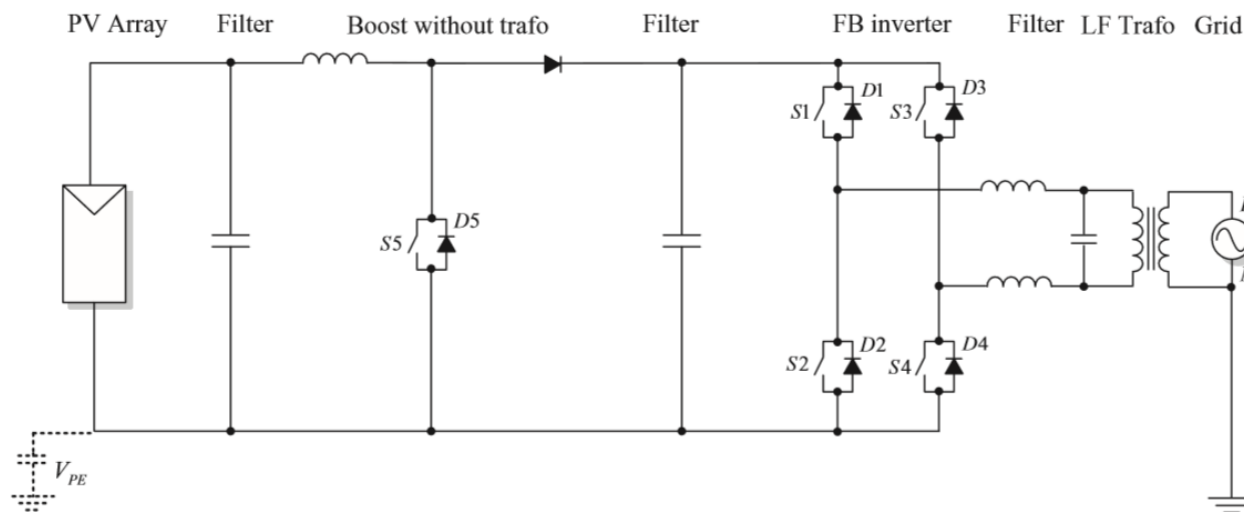


**Figure 2.20** Boosting inverter with a LF transformer based on the boost converter

# SINGLE-PHASE INVERTERS

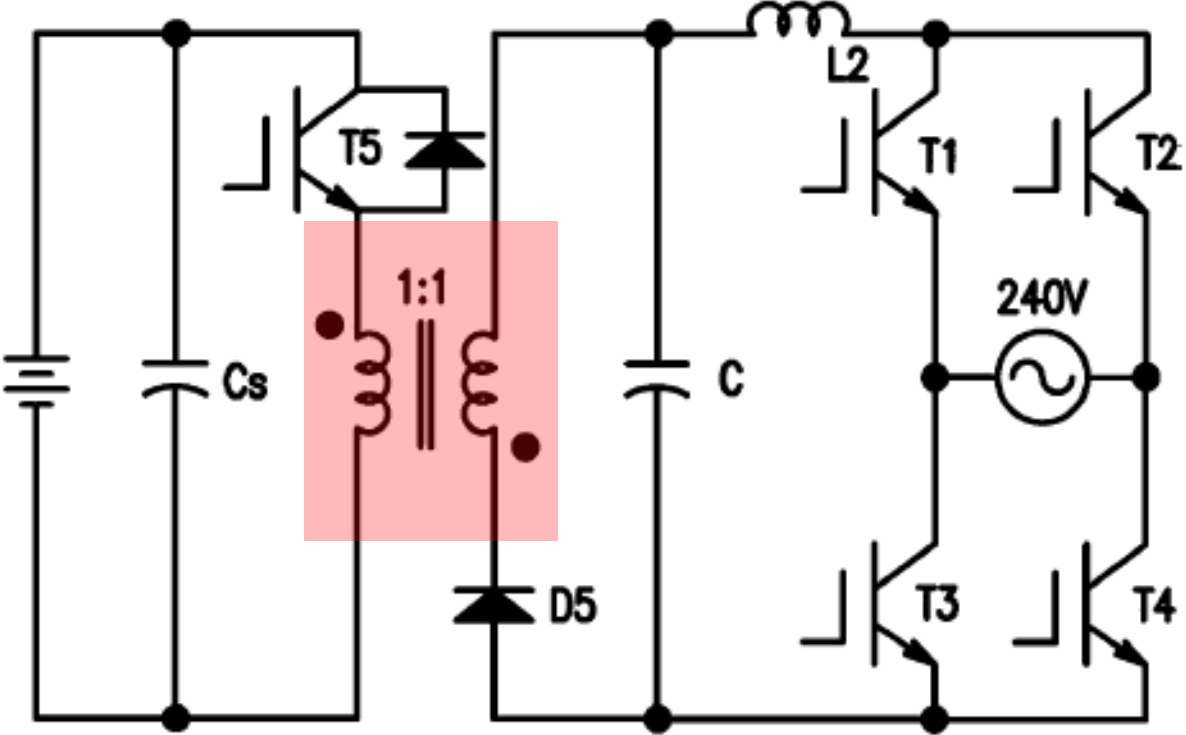

Two-stage isolated buck-boost inverter |


# SINGLE-PHASE INVERTERS

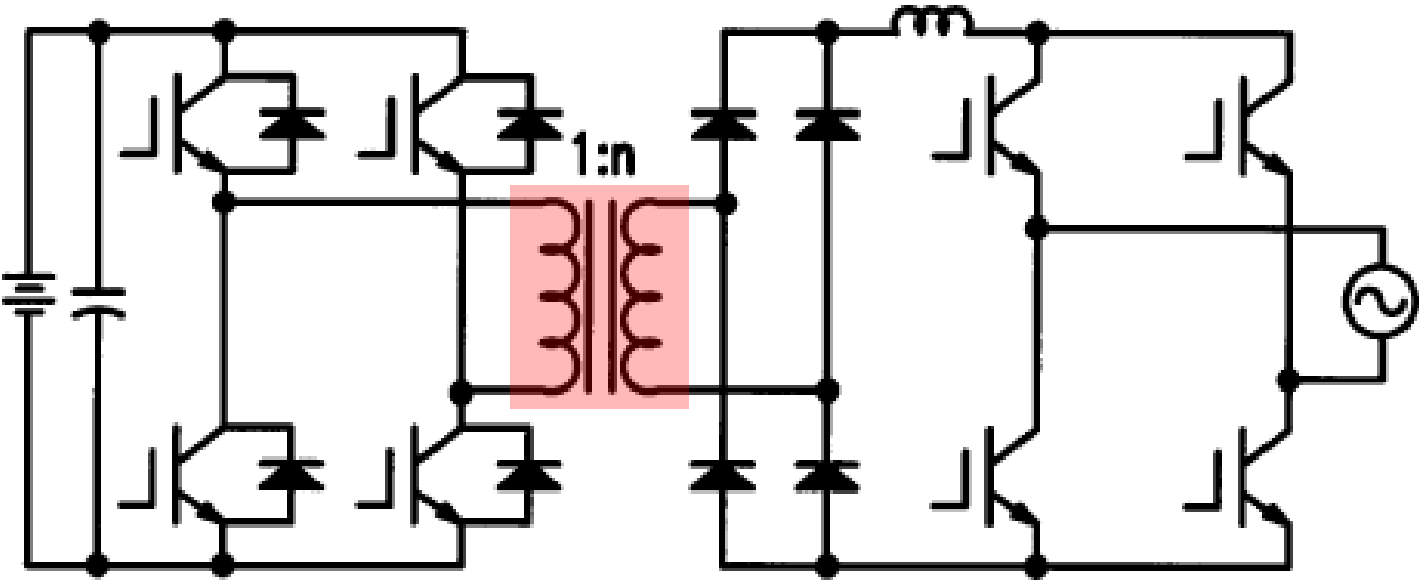


Multiple-stage boost inverter



# SINGLE-PHASE INVERTERS

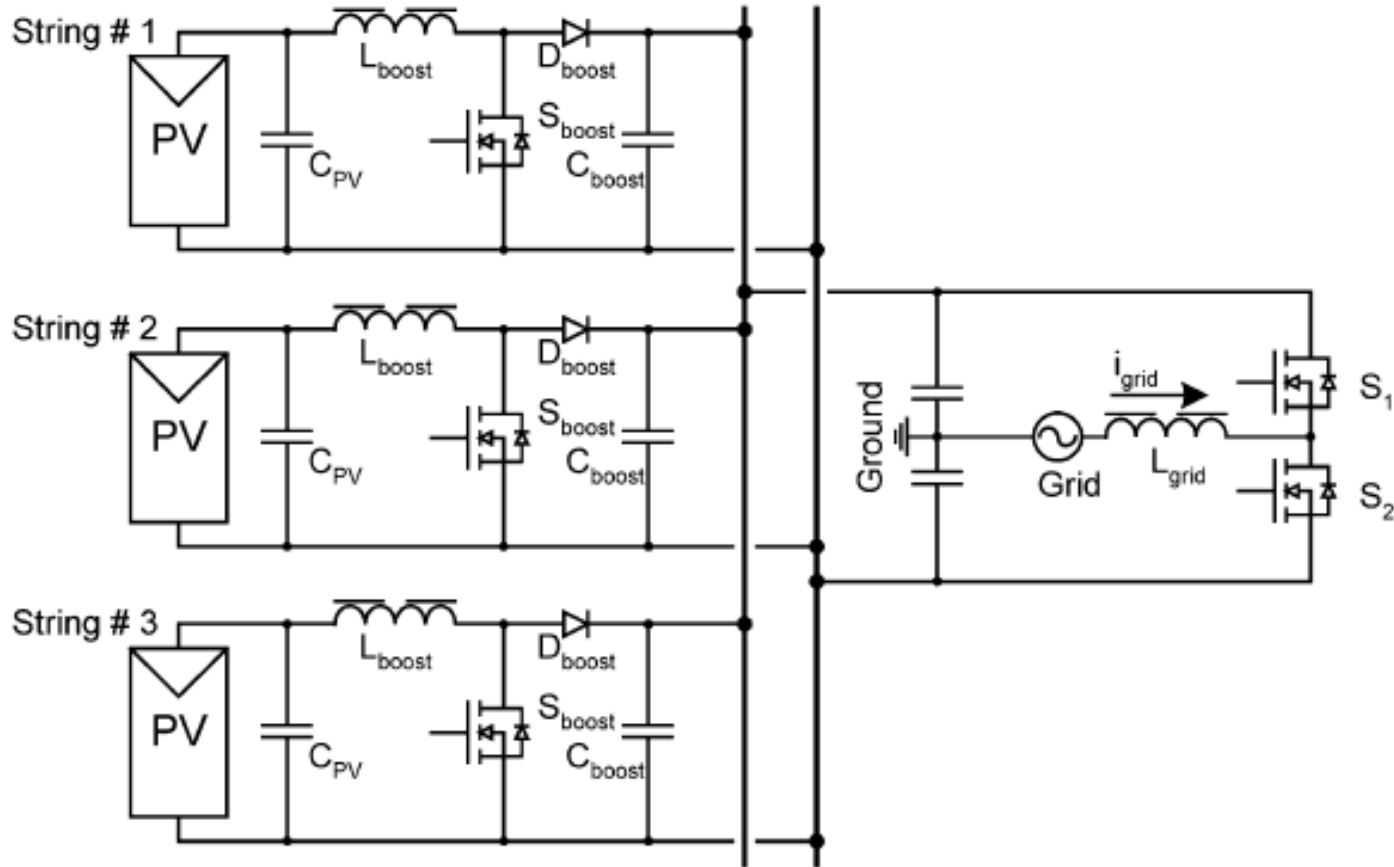


# SINGLE-PHASE INVERTERS

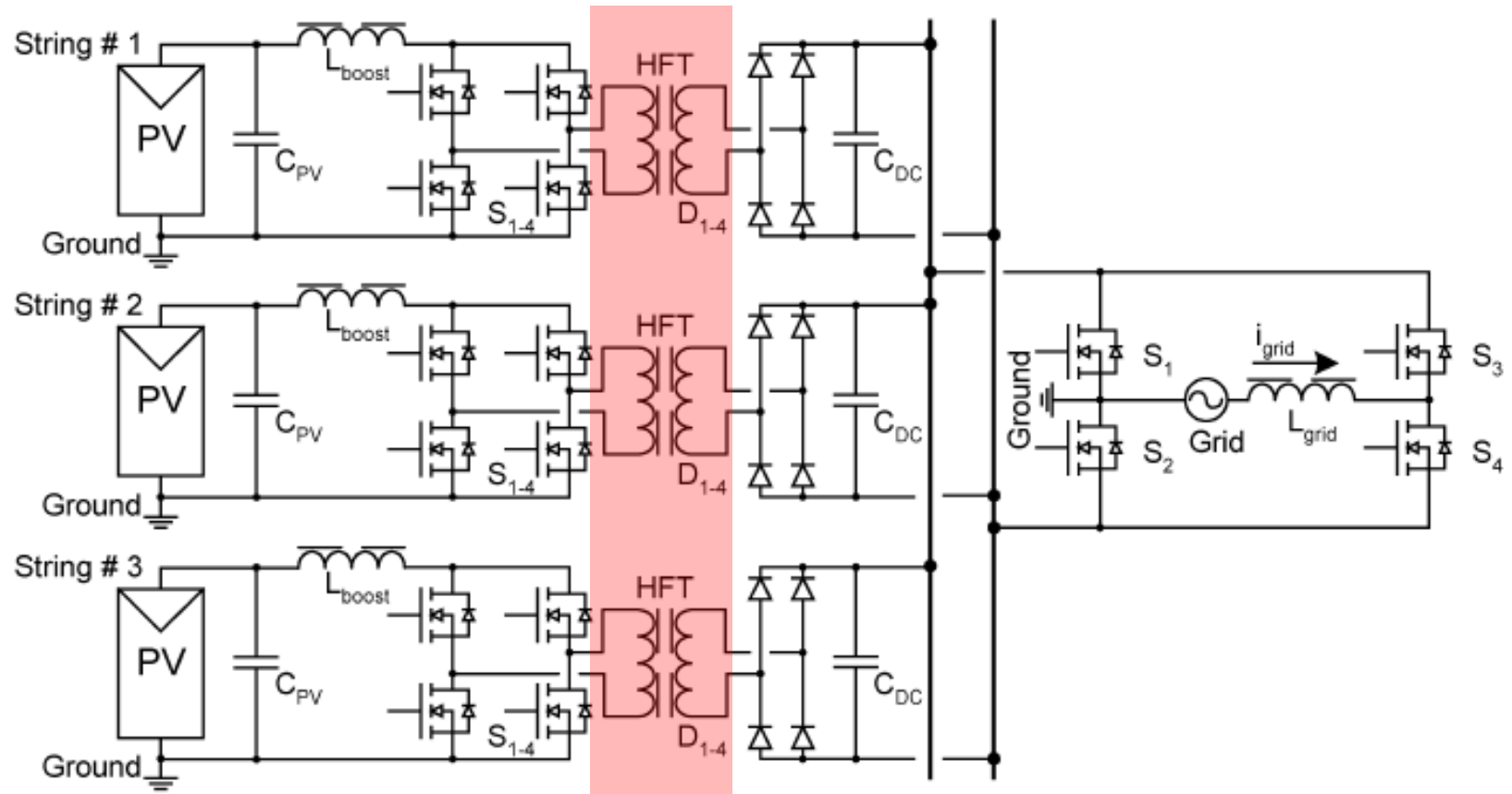

**Remus Teodorescu**  
 Aalborg University, Denmark

**Marco Liserre**  
 Politecnico di Bari, Italy

**Pedro Rodriguez**  
 Technical University of Catalonia, Spain

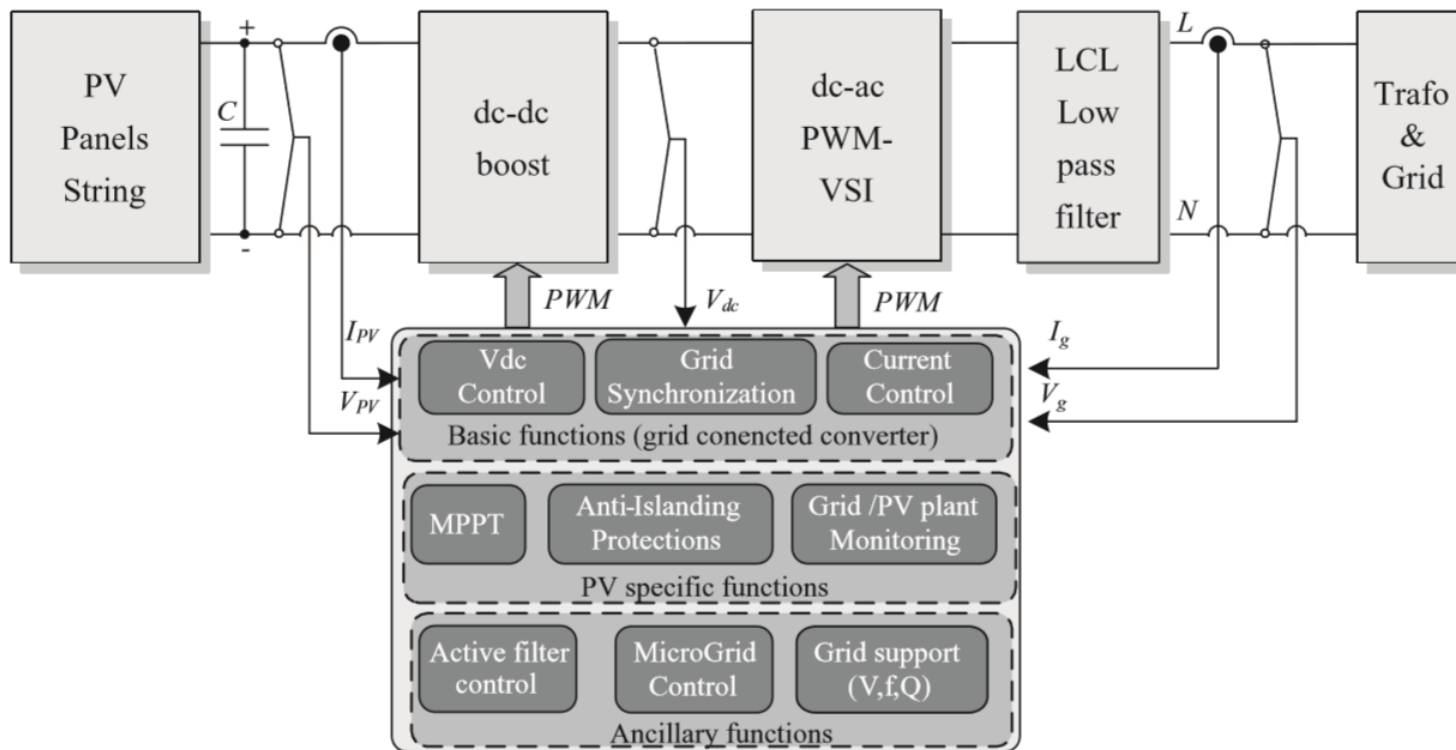

**Figure 2.21** Generic control structure for a PV inverter with boost stage

TABLE I  
SUMMARY OF THE MOST INTERESTING STANDARDS DEALING WITH INTERCONNECTIONS OF PV SYSTEMS TO THE GRID



ISSUE	IEC61727 [3]	IEEE1547 [5]	EN61000-3-2 [4]
Nominal power	10 kW	30 kW	16 A × 230 V = 3.7 kW
Harmonic currents	(3-9) 4.0%	(2-10) 4.0%	(3) 2.30 A
(Order – h) Limits	(11-15) 2.0%	(11-16) 2.0%	(5) 1.14 A
	(17-21) 1.5%	(17-22) 1.5%	(7) 0.77 A
	(23-33) 0.6%	(23-34) 0.6%	(9) 0.40 A
		(> 35) 0.3%	(11) 0.33 A
			(13) 0.21 A
			(15-39) 2.25/h
	Even harmonics in these ranges shall be less than 25% of the odd harmonic limits listed.		Approximately 30% of the odd harmonics -see standard.
Maximum current THD	5.0%		-
Power factor at 50% of rated power	0.90	-	
DC current injection	Less than 1.0% of rated output current.	Less than 0.5% of rated output current.	< 0.22 A -corresponds to a 50 W half-wave rectifier.
Voltage range for normal operation	85% - 110% (196 V – 253 V)	88% - 110% (97 V – 121 V)	-
Frequency range for normal operation	50 ± 1 Hz	59.3 Hz to 60.5 Hz	-

**Design example:**

Using a PWM inverter, DC bus voltage 400 V, inject to the grid (230 Vrms and 50 Hz) a power of 50 W and 20 VA.

questions:

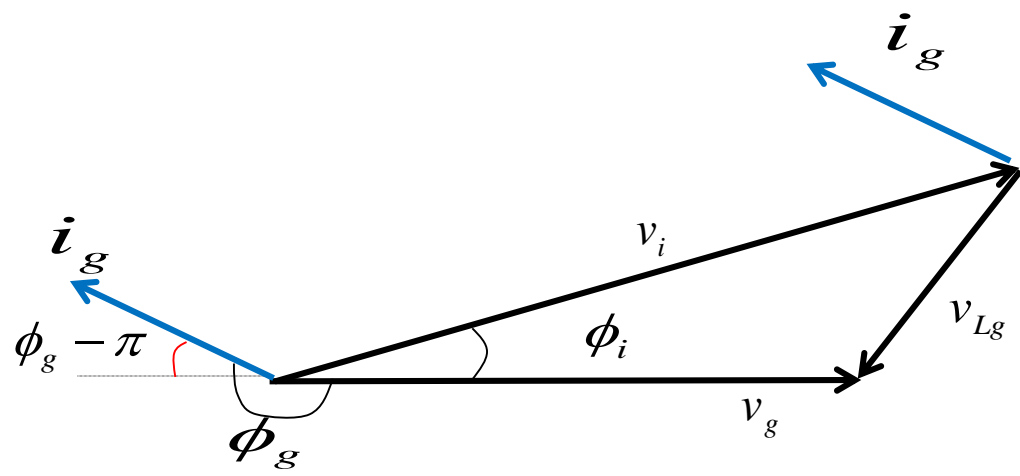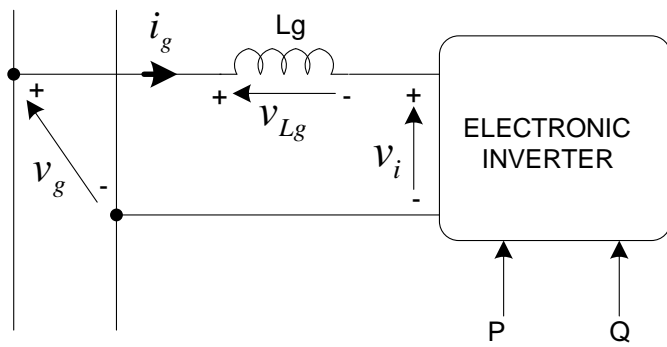
- 1.- Inductance value ( $L_g$ )?
- 2.- Maximum active power (P) and reactive power (Q)?



# EXAMPLE

**P = 50 W**

**Q = 20 VA**

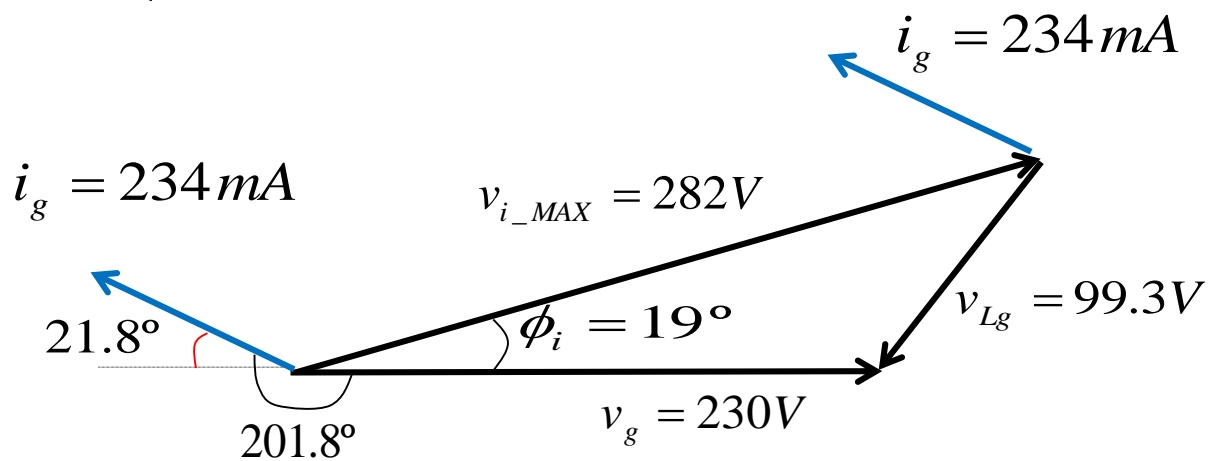

$L_g = 1.35 H$

